

Topic V27

Datapath Building Blocks

Reading: (Section 4.3)


Logic Design Basics

Information encoded in binary

Low voltage = 0, High voltage = 1


One wire per bit

 Multi-bit data encoded on multi-wire buses



Combinatorial


Sequential

 

Combinatorial Elements


AND-gate

$$Y = A \& B$$

 

Multiplexer


$$Y = S ? I1 : I0$$

 

Combinatorial Elements


AND-gate

$$Y = A \& B$$

 


Adder

$$Y = A + B$$

 


Multiplexer

$$Y = S ? I1 : I0$$

 

Arithmetic/Logic Unit


$$Y = F(A, B)$$

 


Sequential Elements: Register

Stores data in a circuit

 Uses a Clock signal to determine when to update the stored value





 Edge-triggered: update when Clock changes from 0 to 1



Register with Write Control

  Only updates on clock edge
when write control input is 1




Clocking Methodology

Combinational logic transforms data during clock cycles

Between clock edges

Input from state elements, output to state element

Longest delay determines clock period

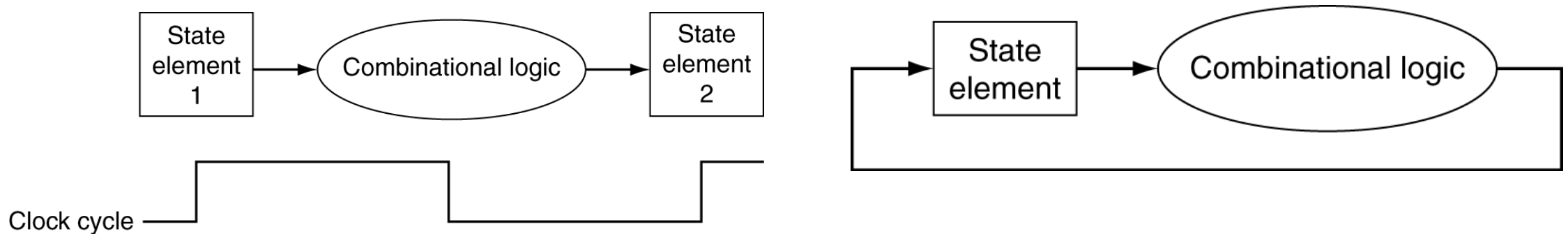

Building a Datapath

Datapath


Processes data and addresses in the CPU

Registers, ALUs, muxes, memories, ...


We will build a RISC-V Datapath incrementally

Refining the overview design



Datapath: Instruction Memory

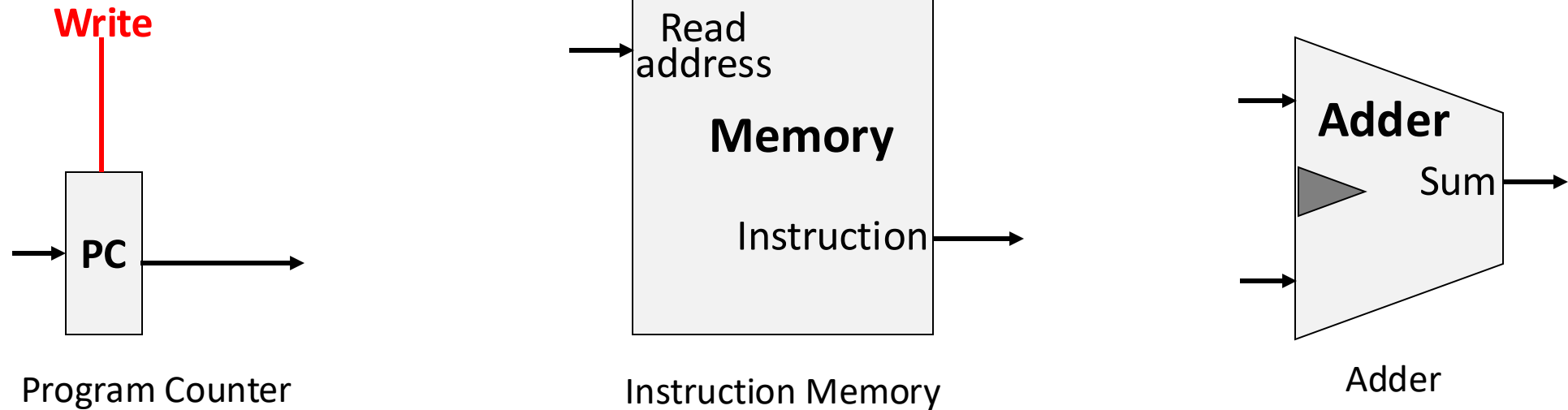


Datapath: PC Incrementor

 


Datapath: Register File and ALU

 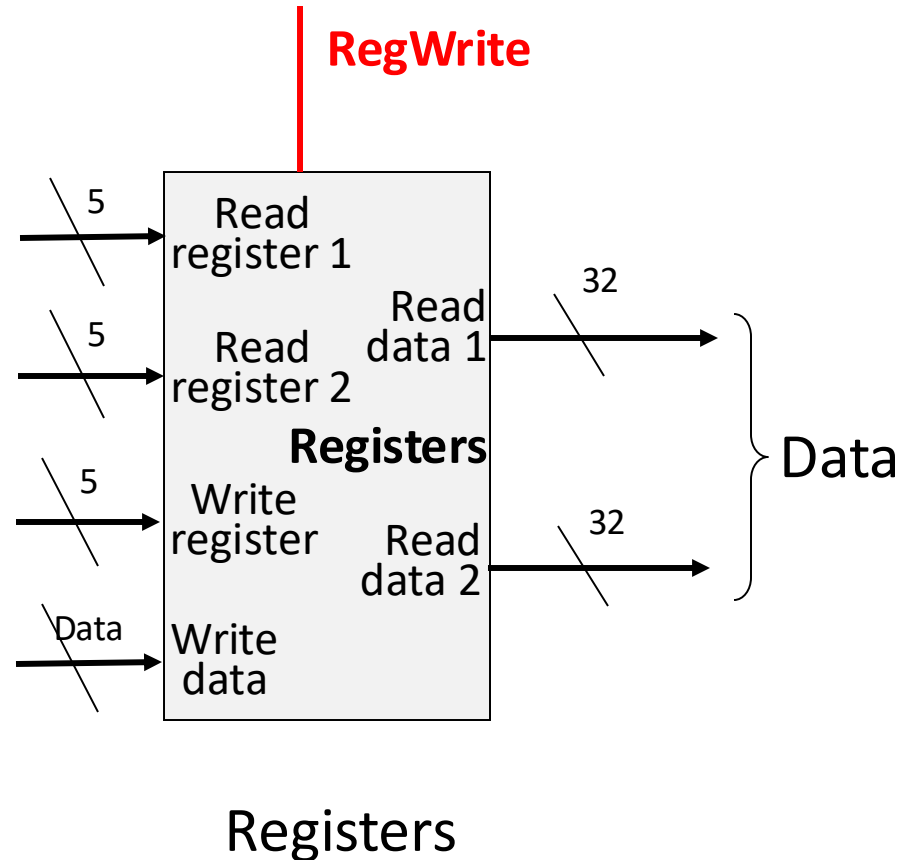

A Two Read Port File with n Registers

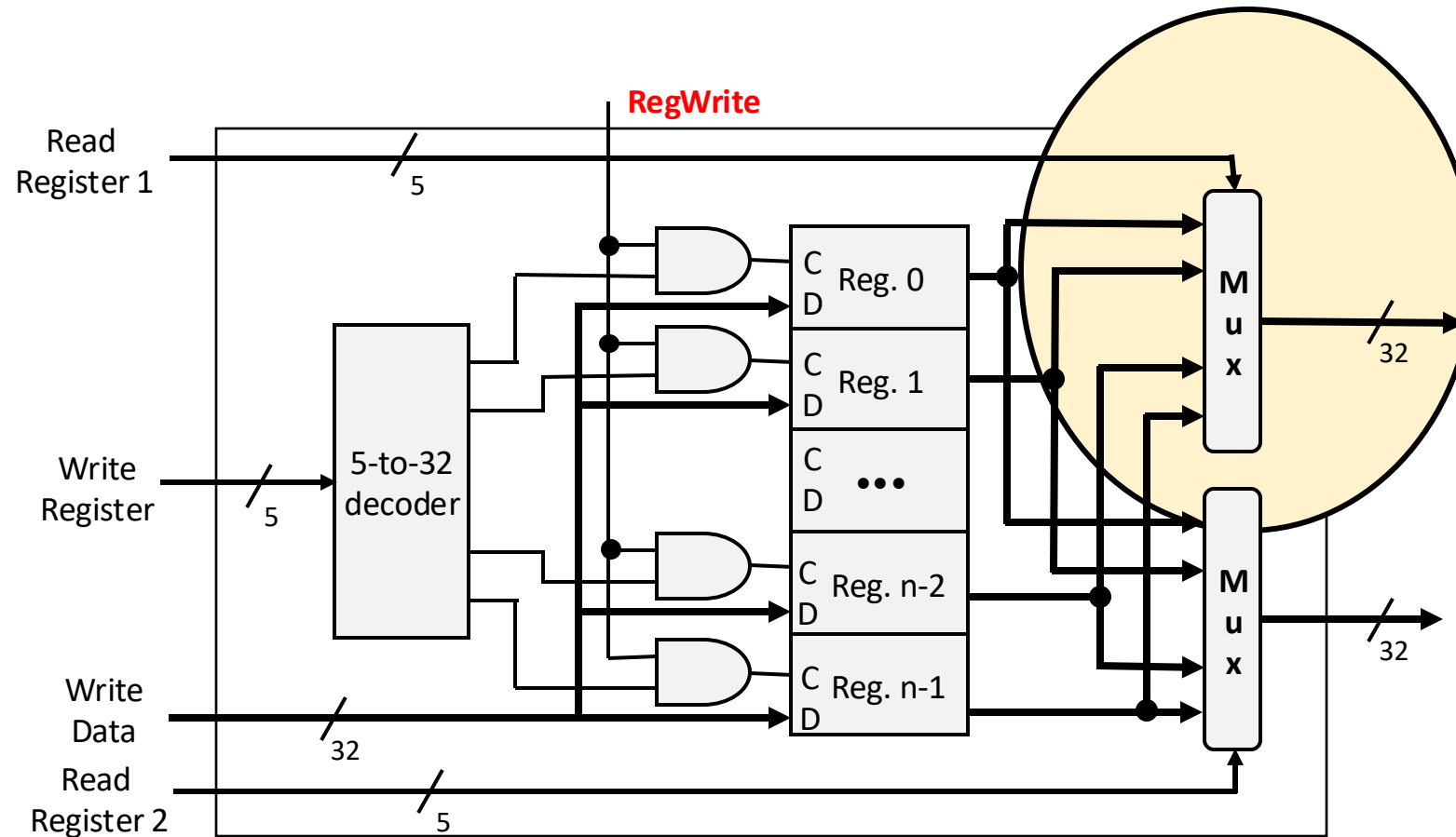

Read
Register 1

 

Read
Register 1

