


# Topic V2B

Pipelined Datapath

Readings: (Sections 4.6-4.7)

# RISC-V Pipelined Datapath


Signals flow  
left-to-right

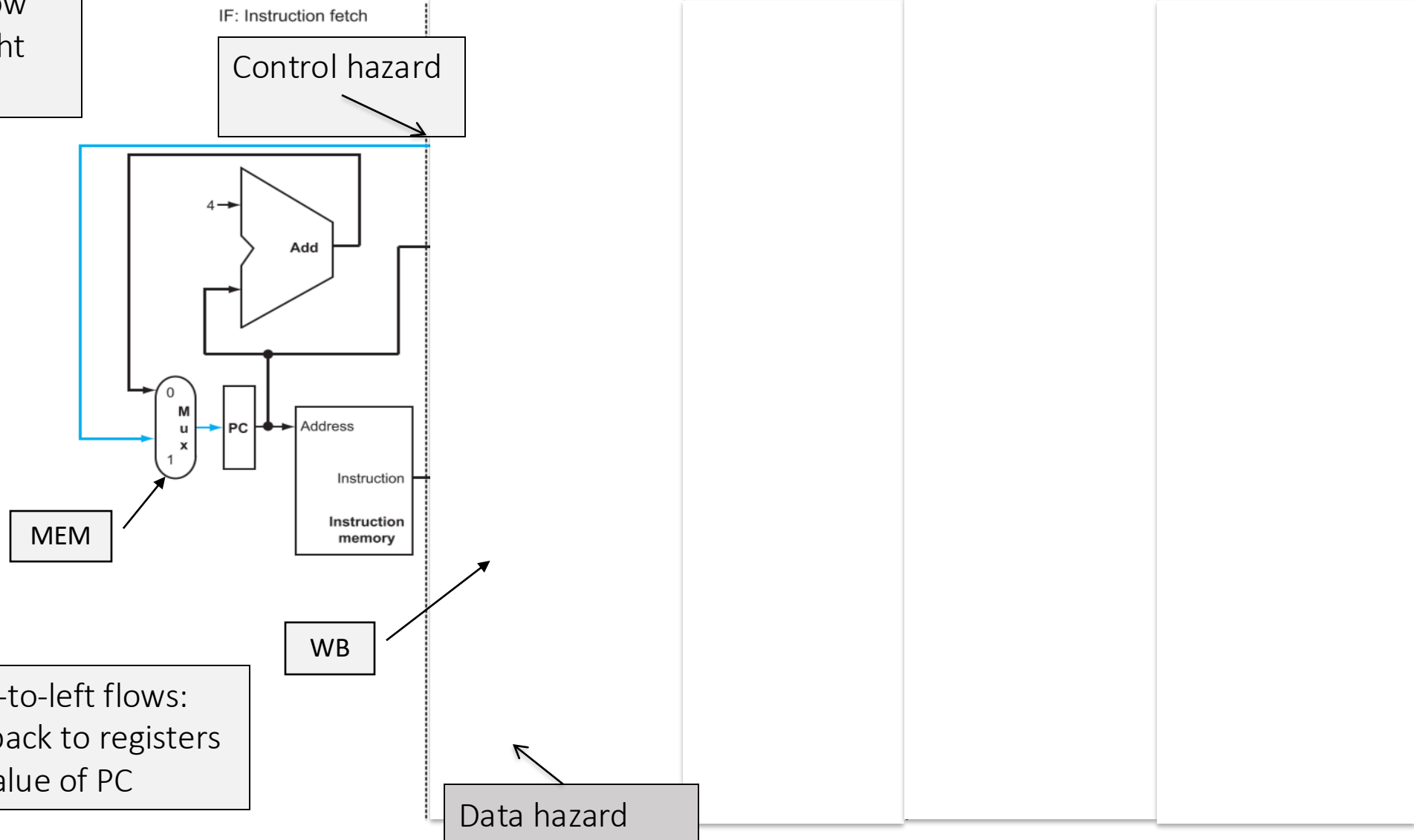

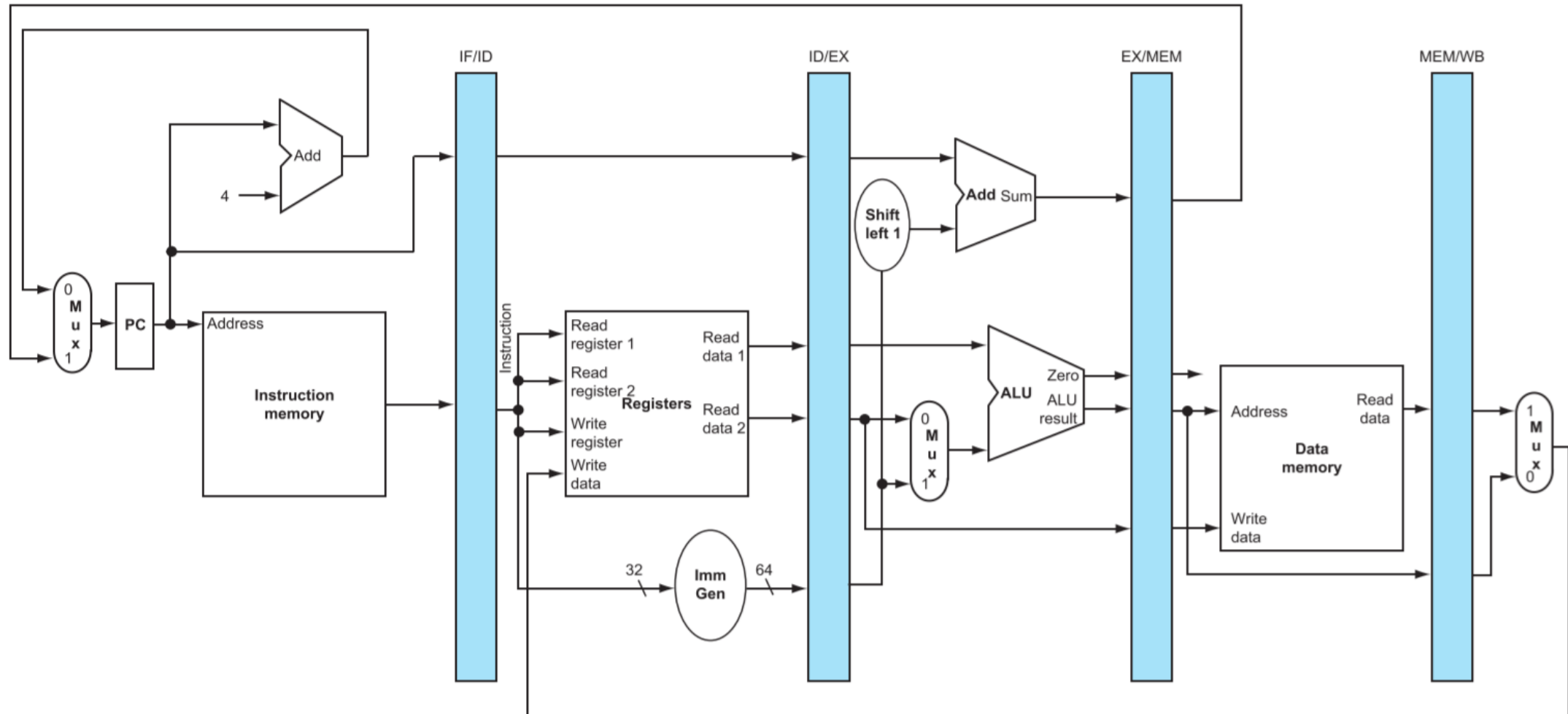
# Pipeline registers

Need registers between stages


To hold information produced in previous cycle




# Instr. Fetch (IF) for Load, Store, ...

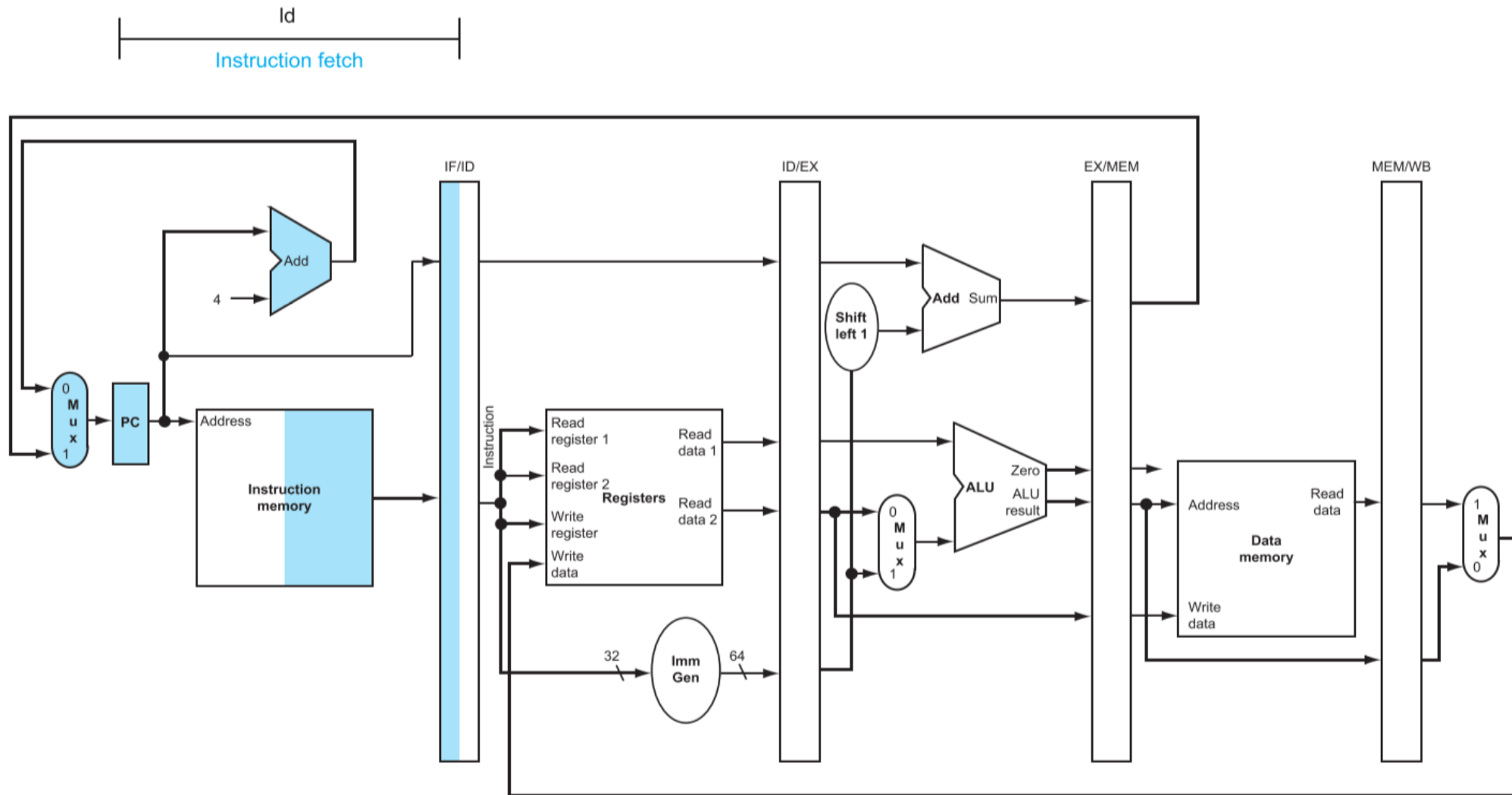

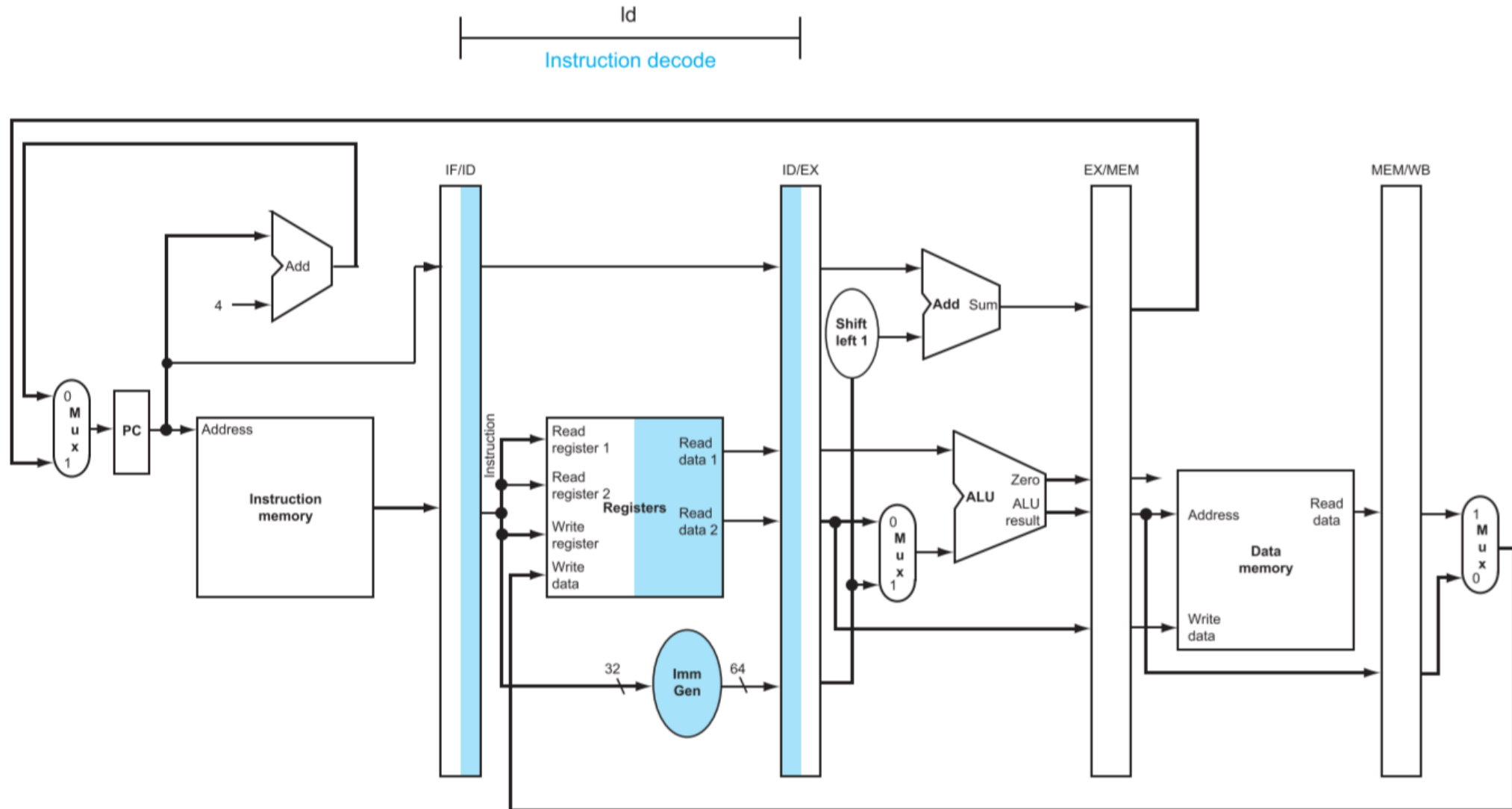
# Instr. Decode (ID) for Load, Store, ...




# Execution (EX) for Load

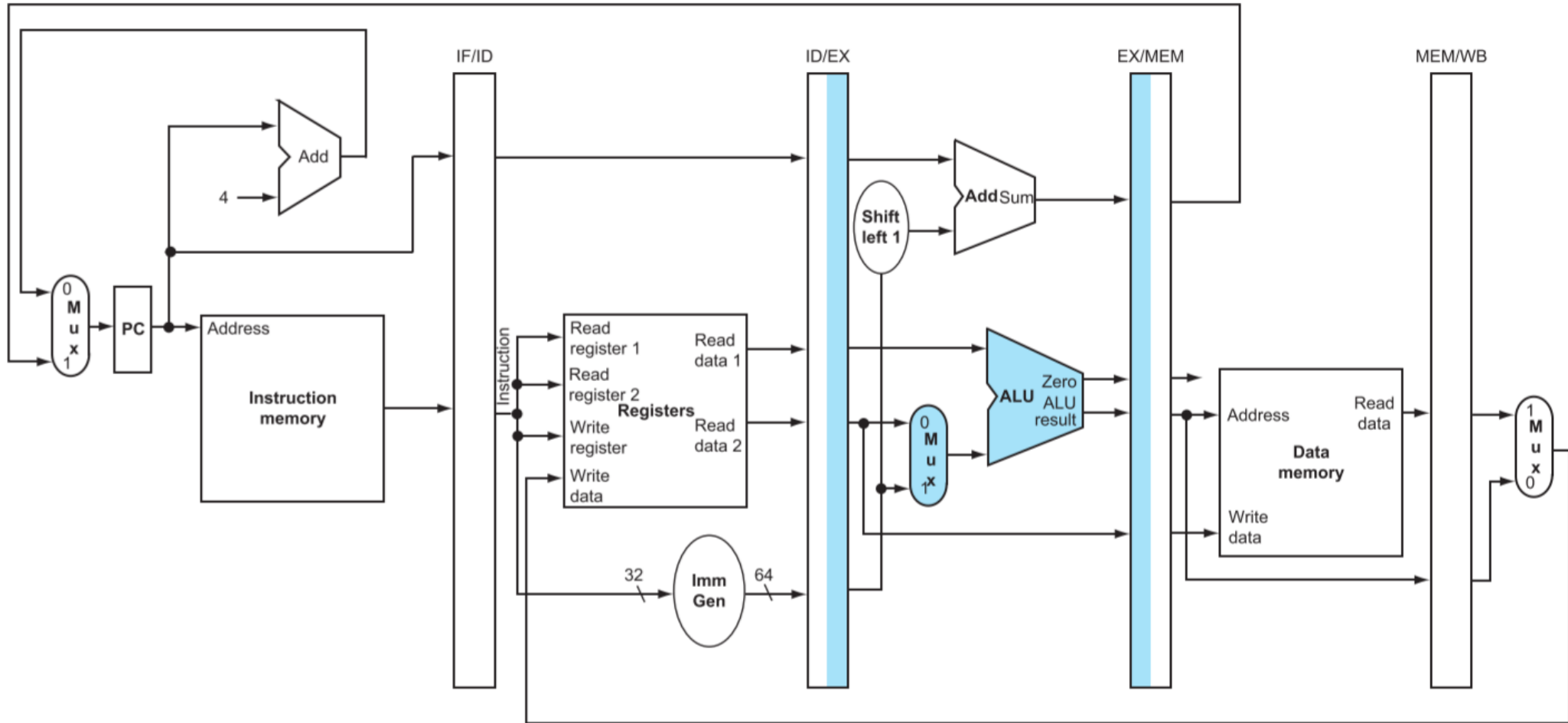

# Memory (MEM) for Load

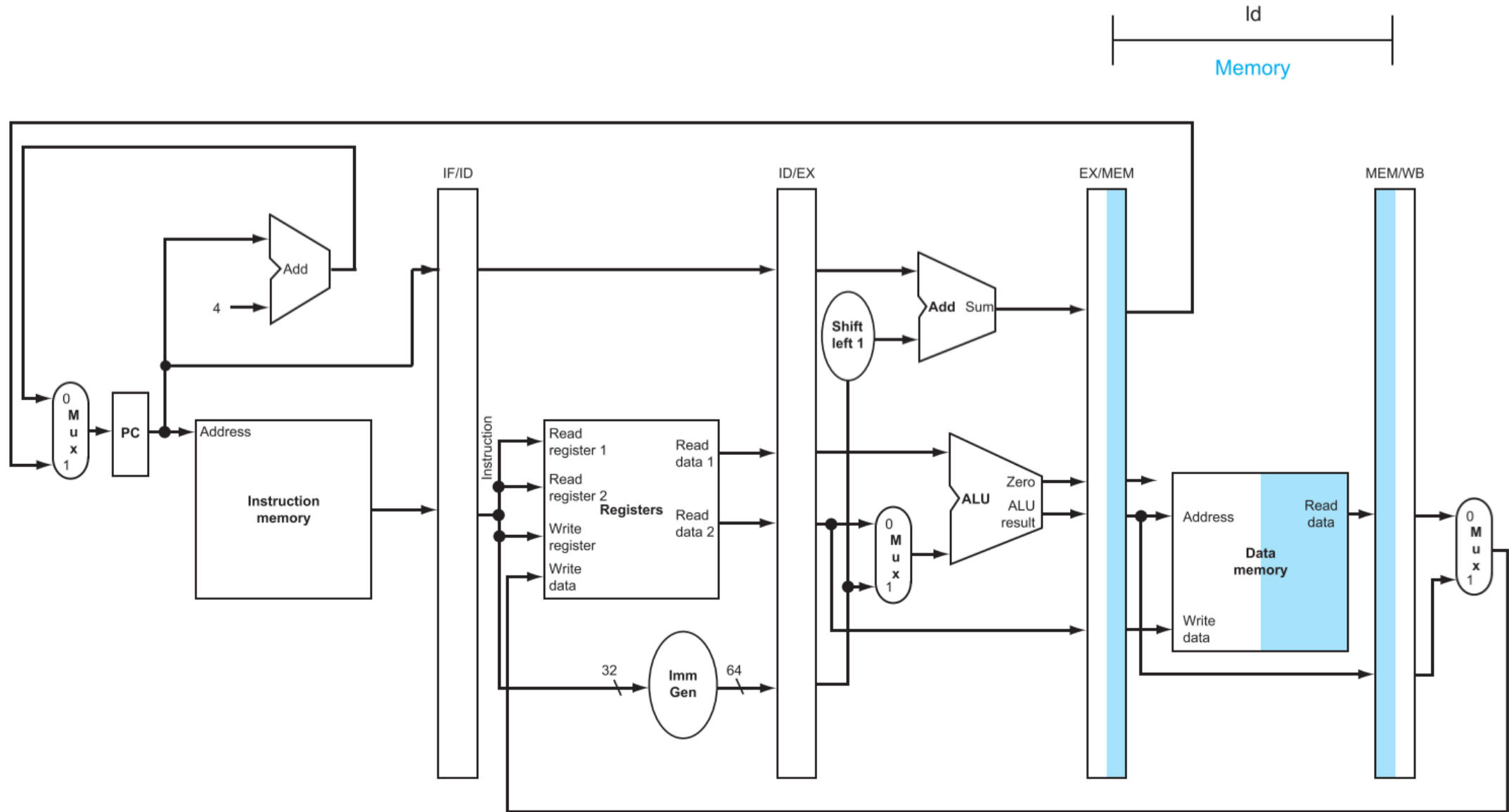


# Write Back (WB) for Load

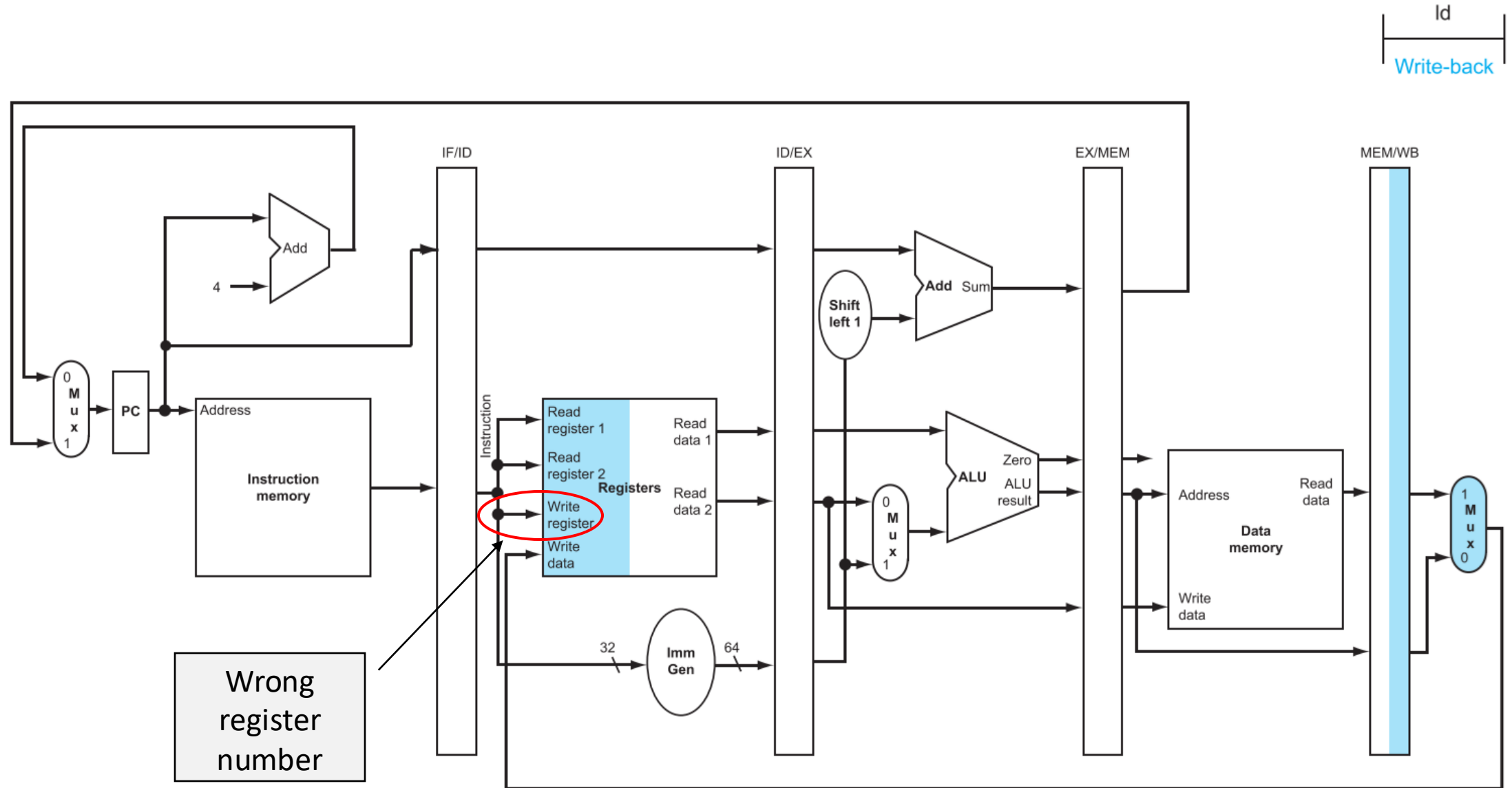




# Corrected Datapath for Load

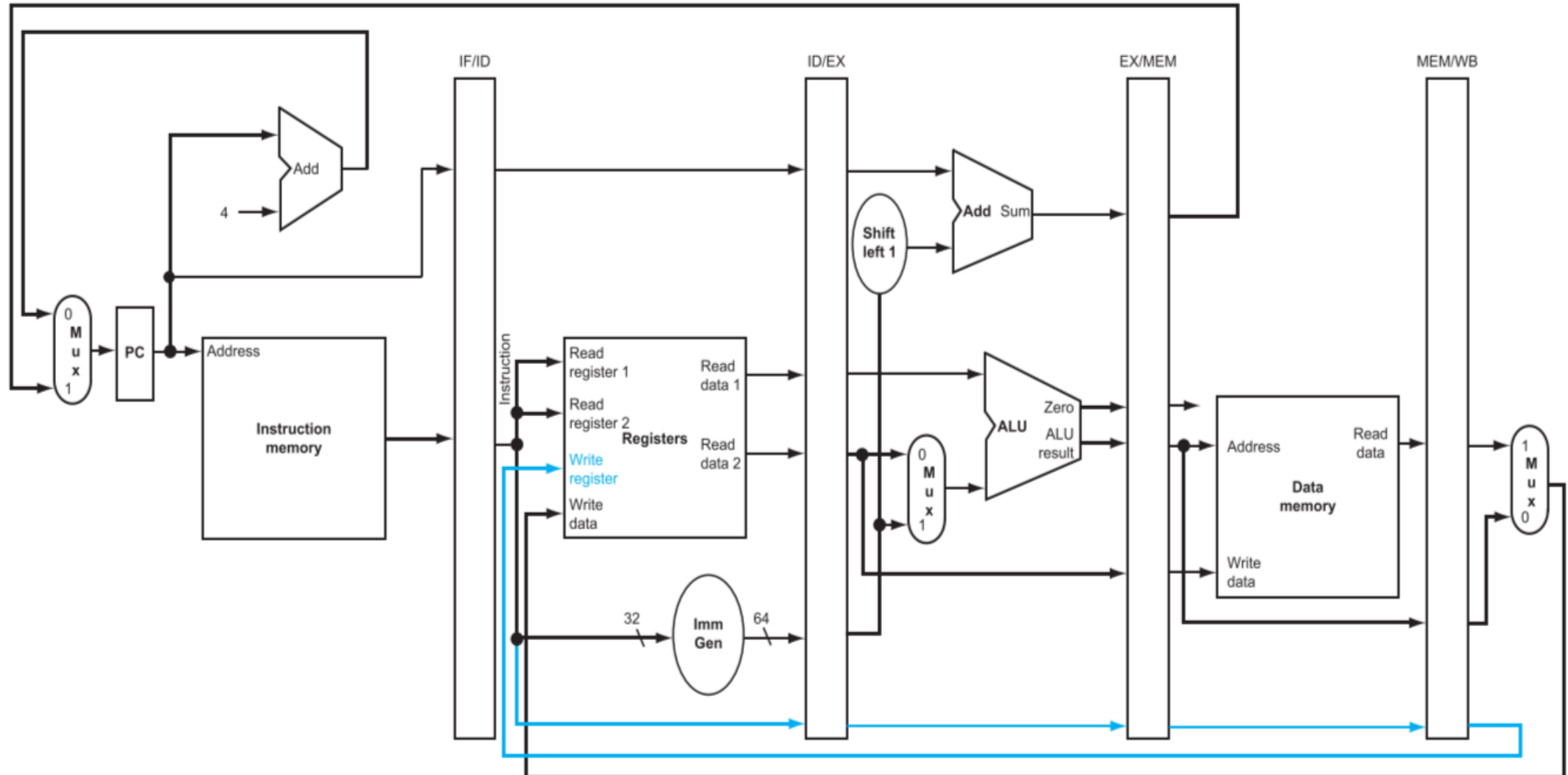


Snapshot of Pipeline State in a given Cycle

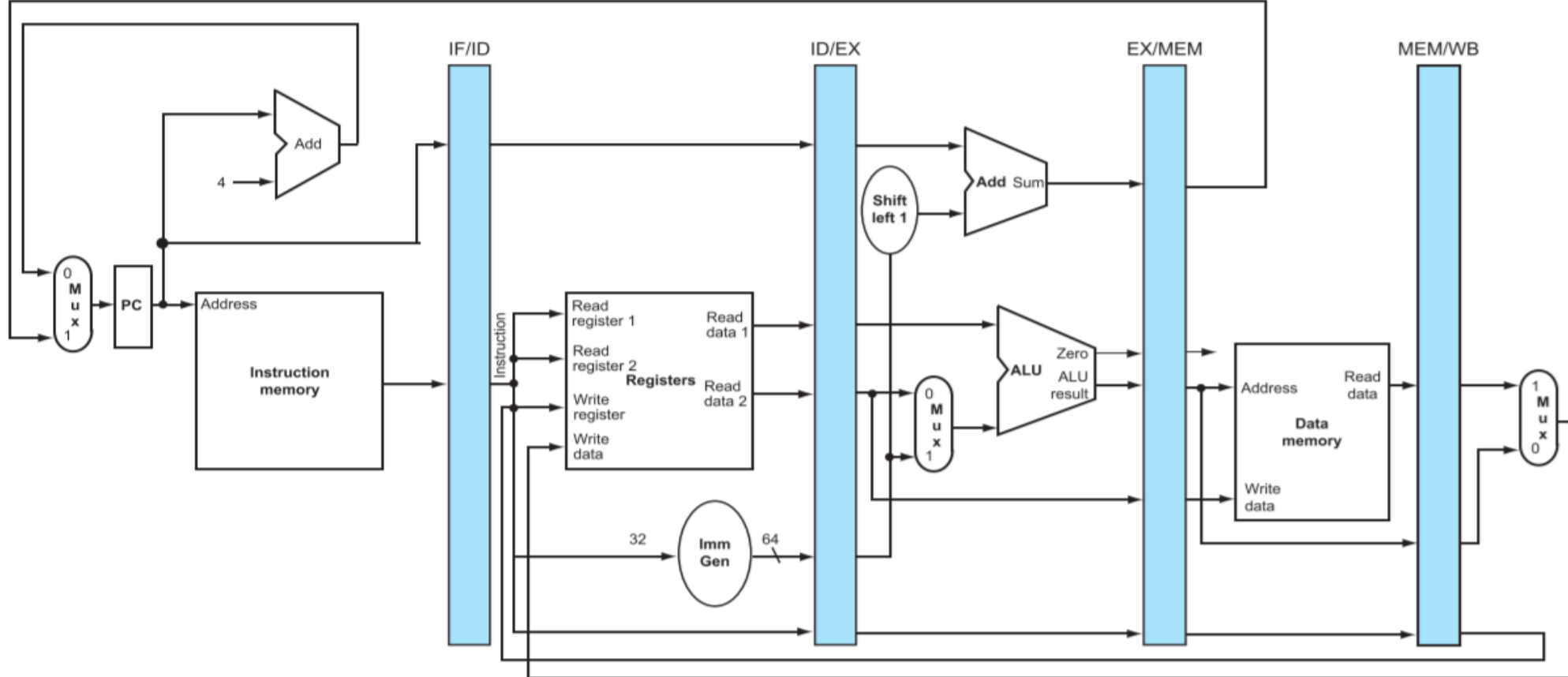ld x10, 40(\$1) ●  
 sub x11, x2, x3 ●  
 add x12, x3, x4 ●  
 ld x13, 48(x1) ●  
 add x14, x5, x6 ●




# Pipelined Control (Simplified)

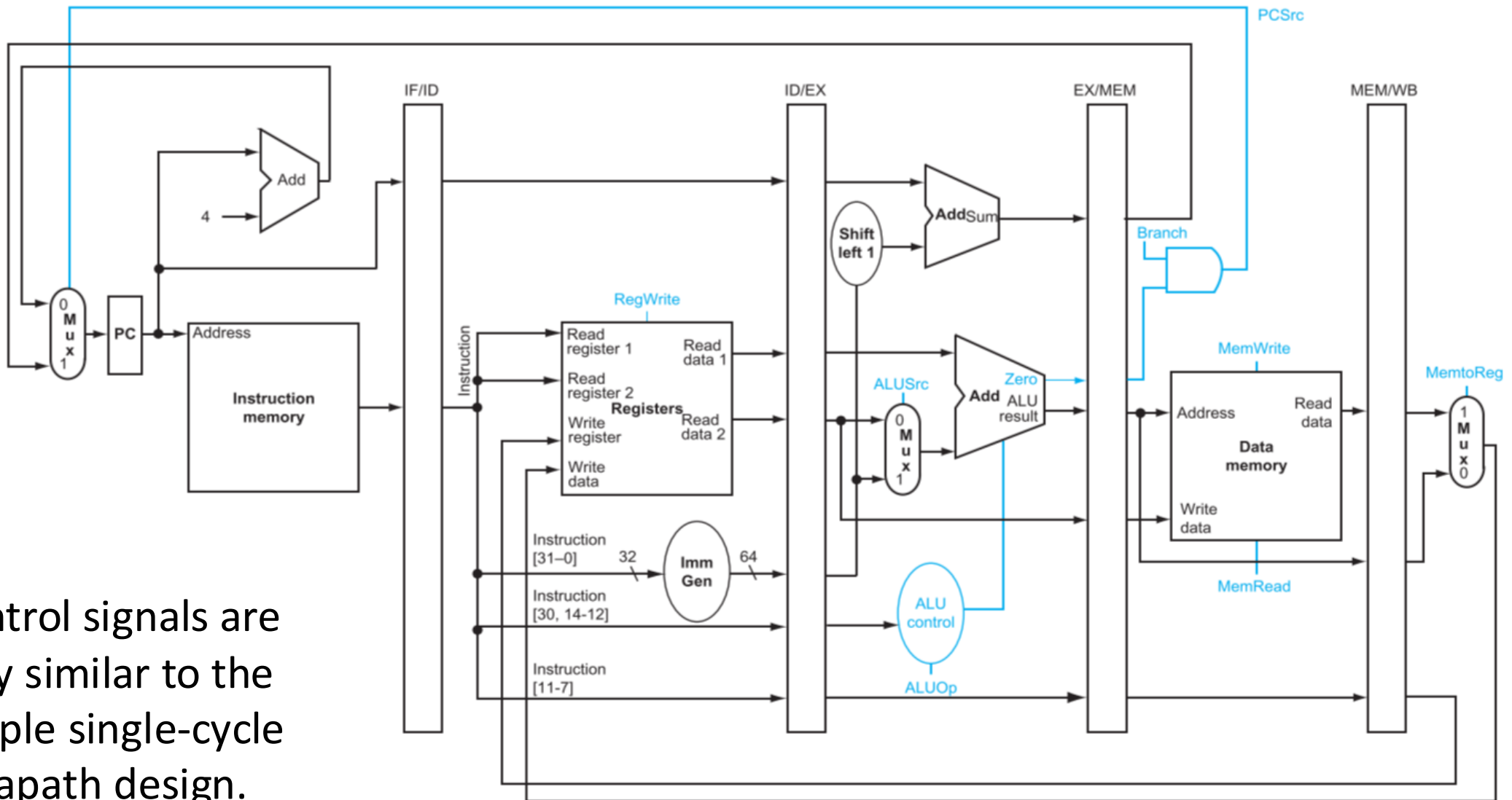

Control signals are very similar to the simple single-cycle datapath design.
 
# Pipelined Control


Control signals derived from instruction  
As in single-cycle implementation



All control signals  
are created in the  
decode stage.

Inter-stage registers  
only need to store  
control signals that  
will be used later.

# Pipelined Control

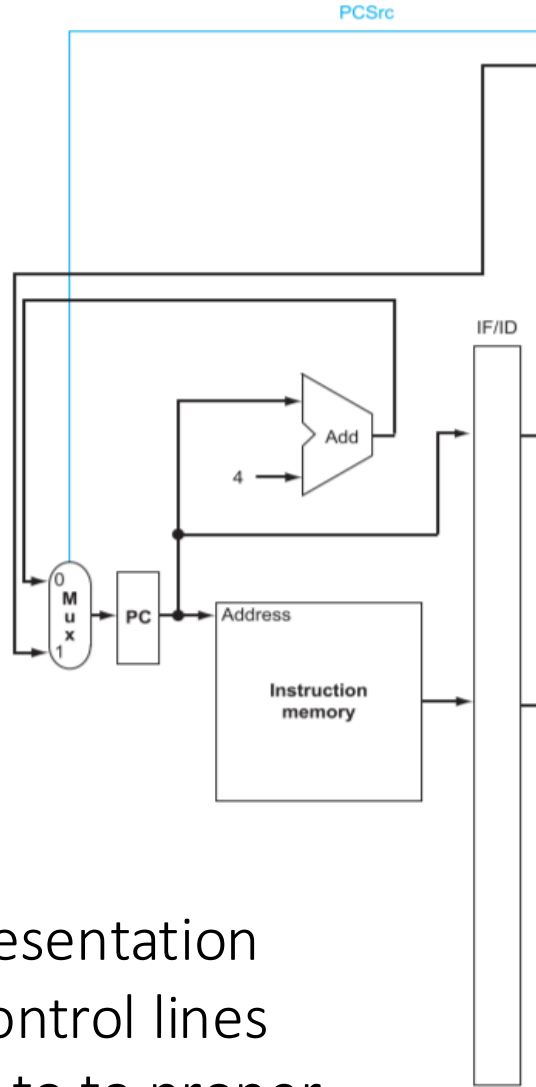


Same representation  
but with control lines  
connected to proper  
stages.

# Data Hazards in ALU Instructions

sub **x2**, x1, x3      sub  
 and x12, **x2**, x5      and  
 or x13, x6, **x2**      or  
 and x14, **x2**, **x2**      and  
 sw x15, 200(**x2**)      sw


x2 = 10 here  
 x2 = -20 here

## Without Forwarding

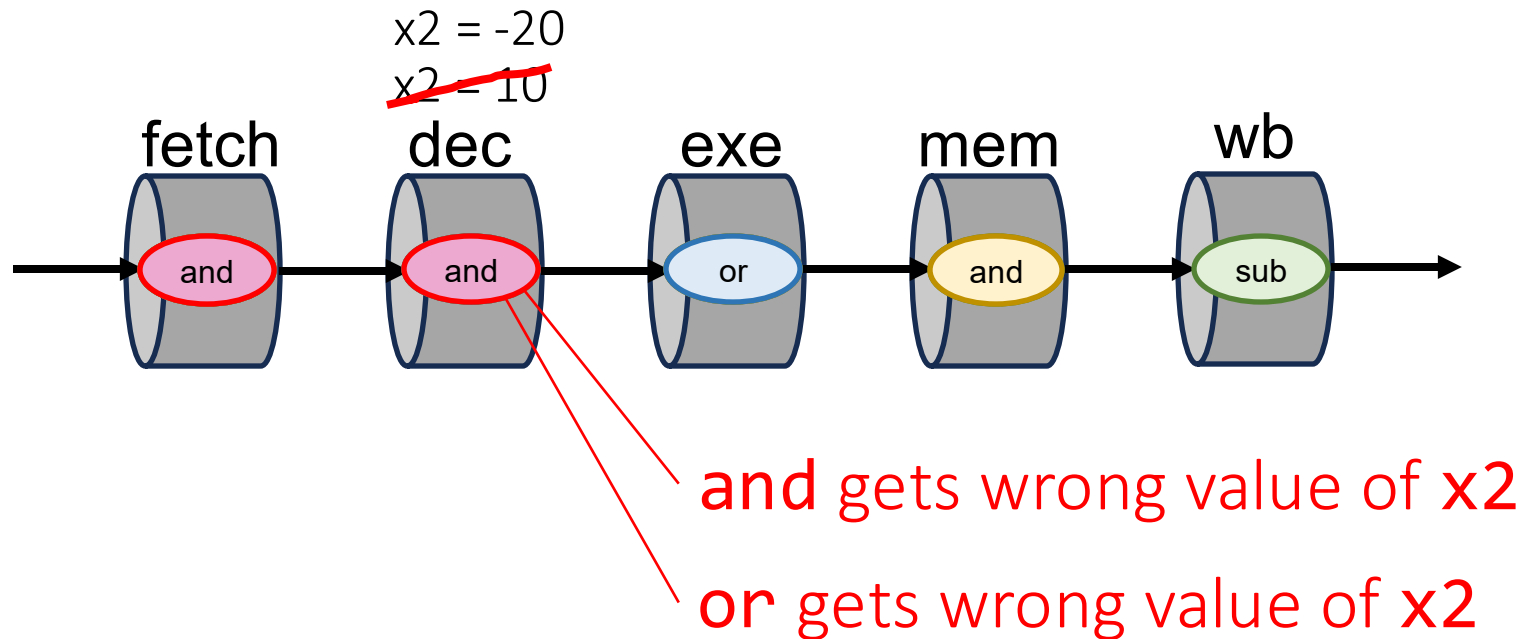



# With Forwarding

 


# RISC-V Forwarding Unit Logic

How RISC-V detects that forwarding is needed?

Example: forwarding to EX stage


Only need to forward if instruction in EX  
writes to a register.

And only if  $Rd \neq x0$

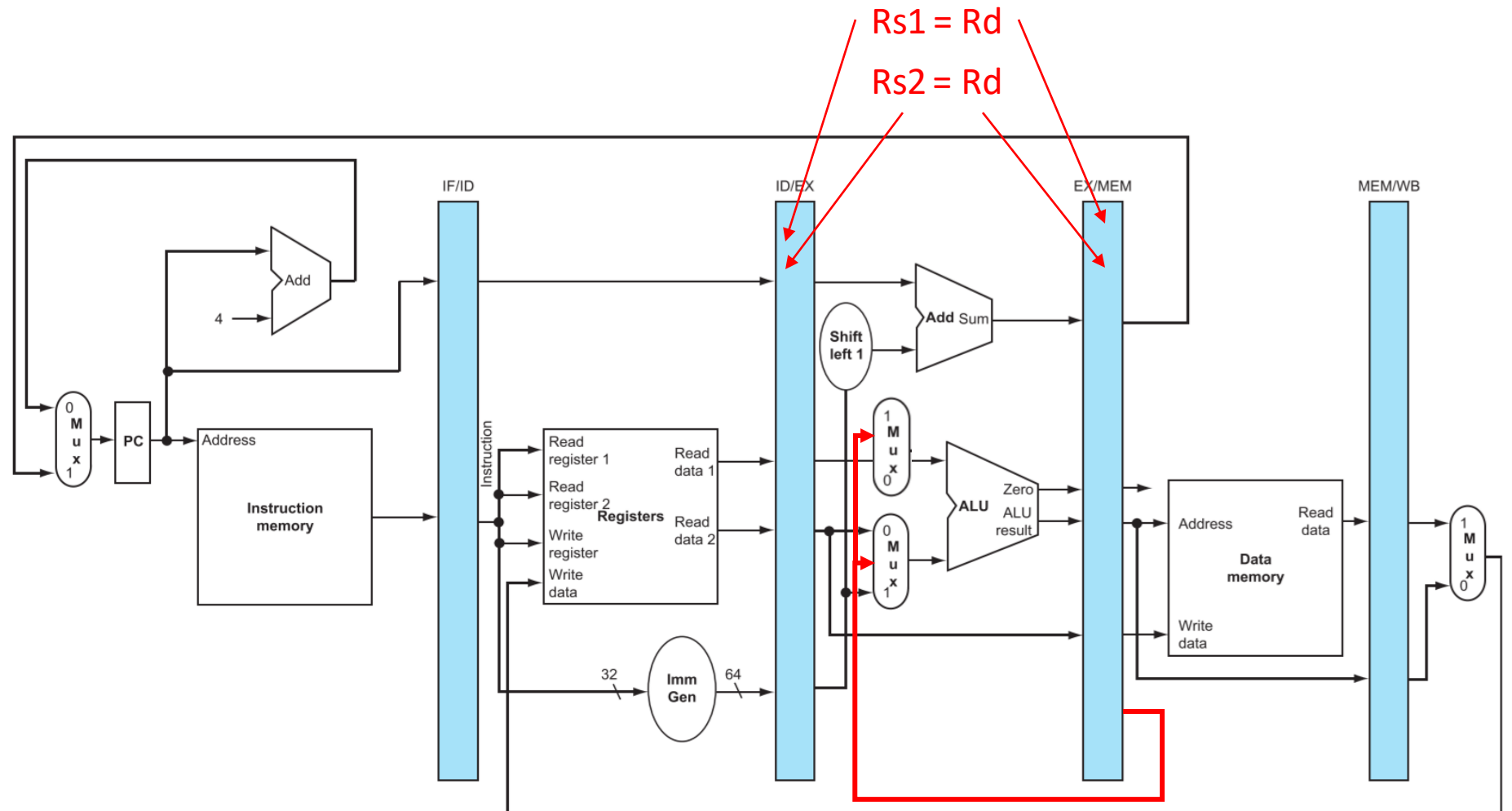


Only need to forward if instruction in MEM  
writes to a register.

And only if  $Rd \neq x0$

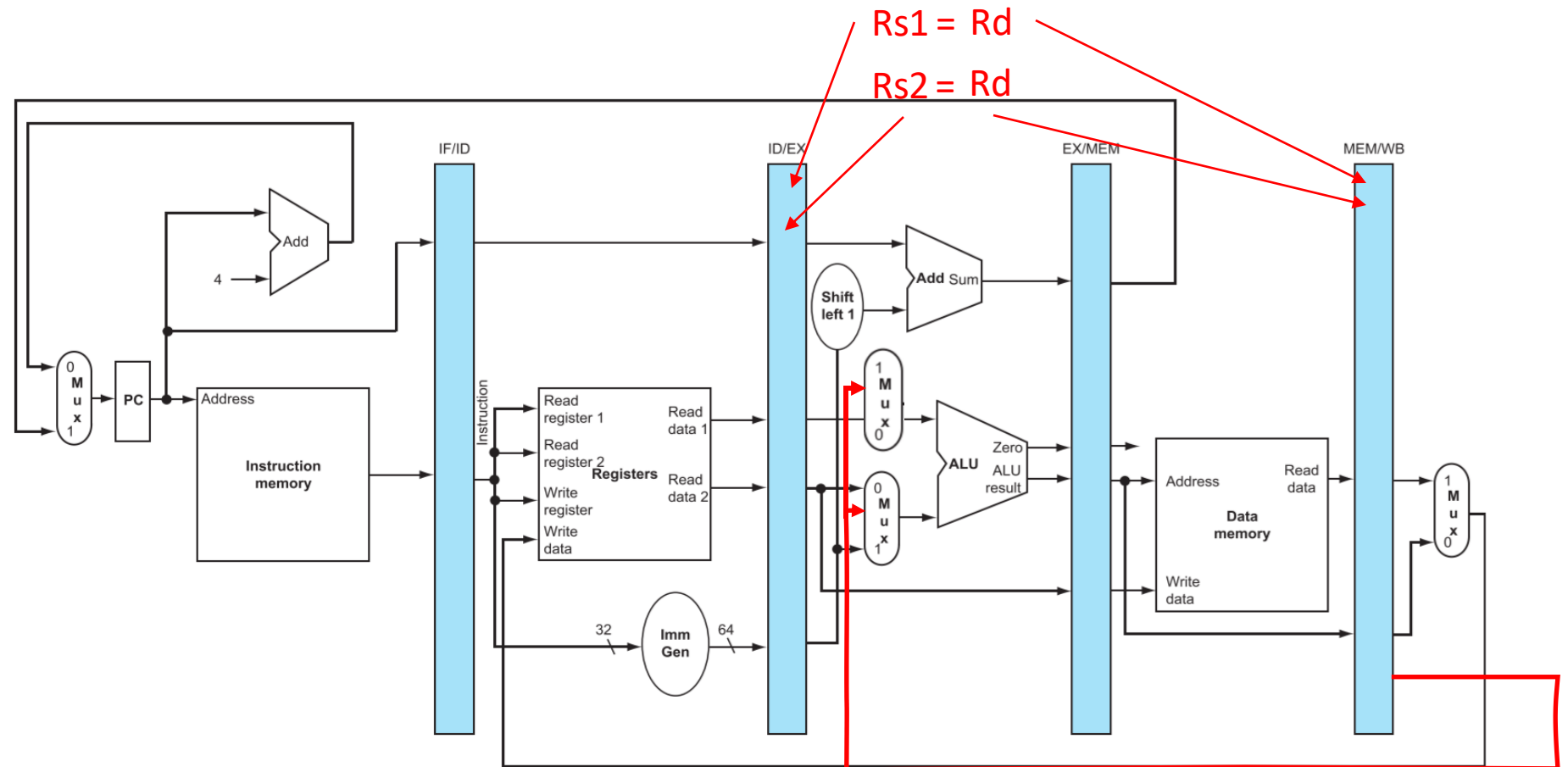


# Forwarding Paths

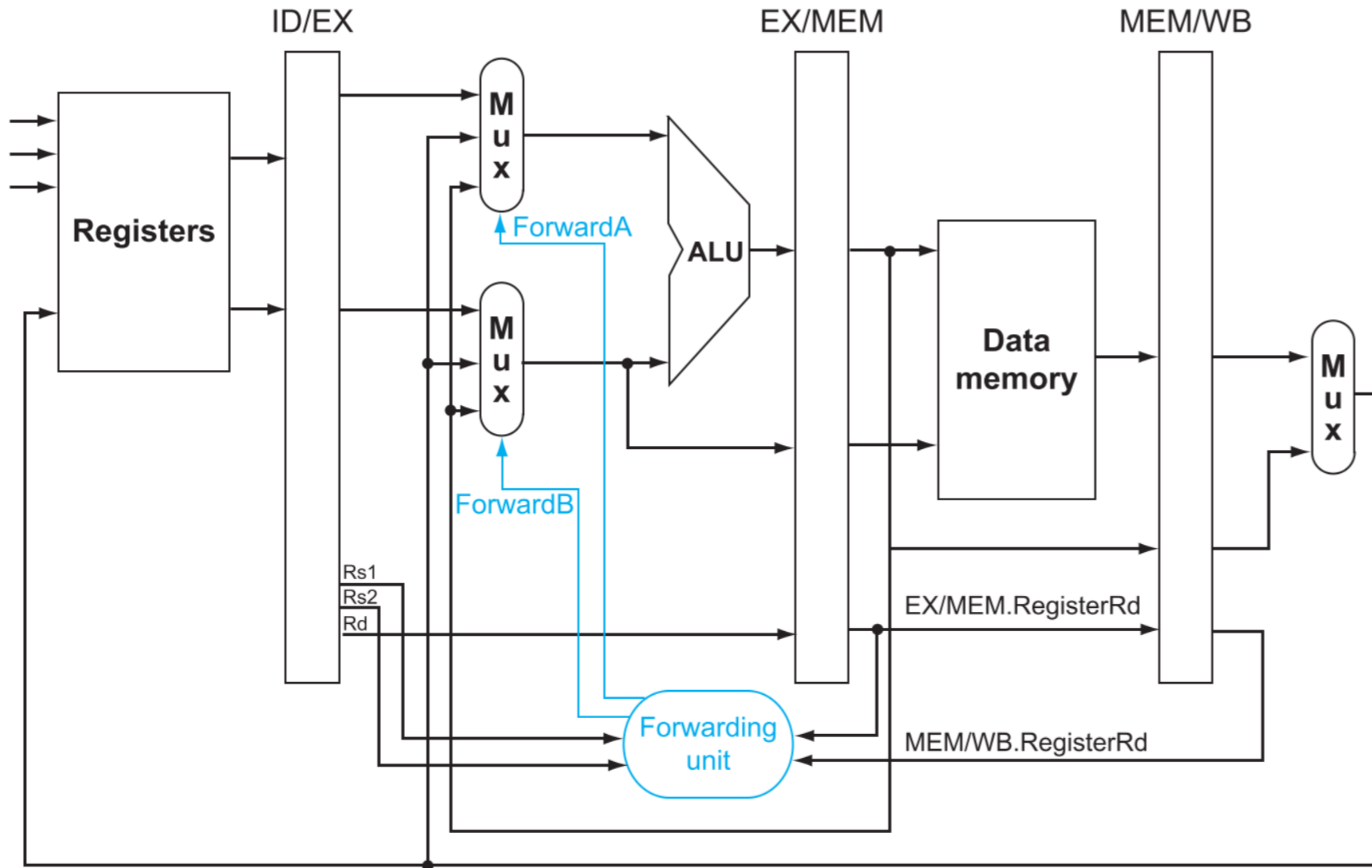

b. With forwarding

# When a load/use stall is needed?

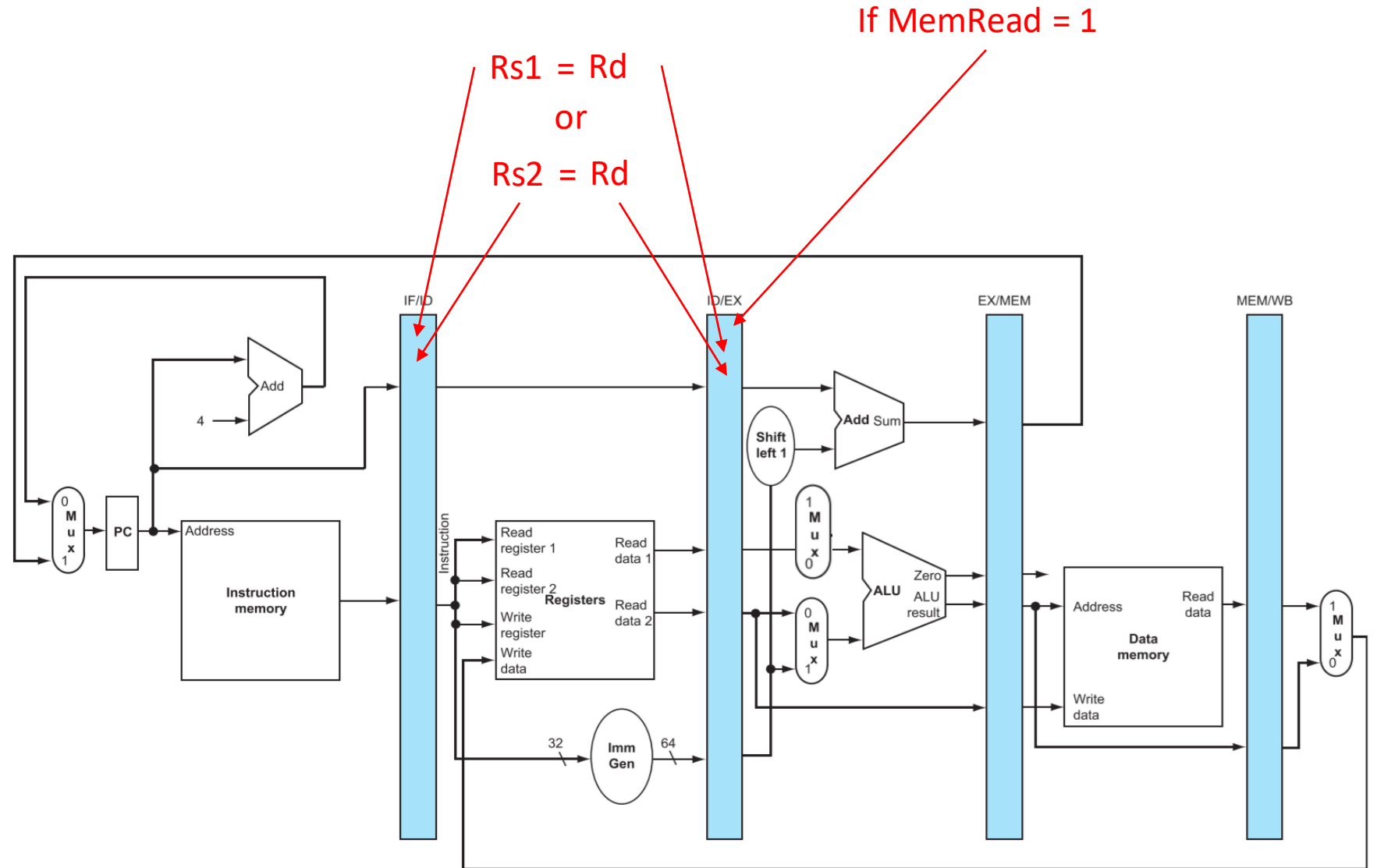


How to Stall the Pipeline?

Change PC to fetch the instruction in IF again.


Force all control lines in ID/EX to 0:  
EX, MEM, WB will execute nop (no operation)

Repeat decoding of Instruction in ID

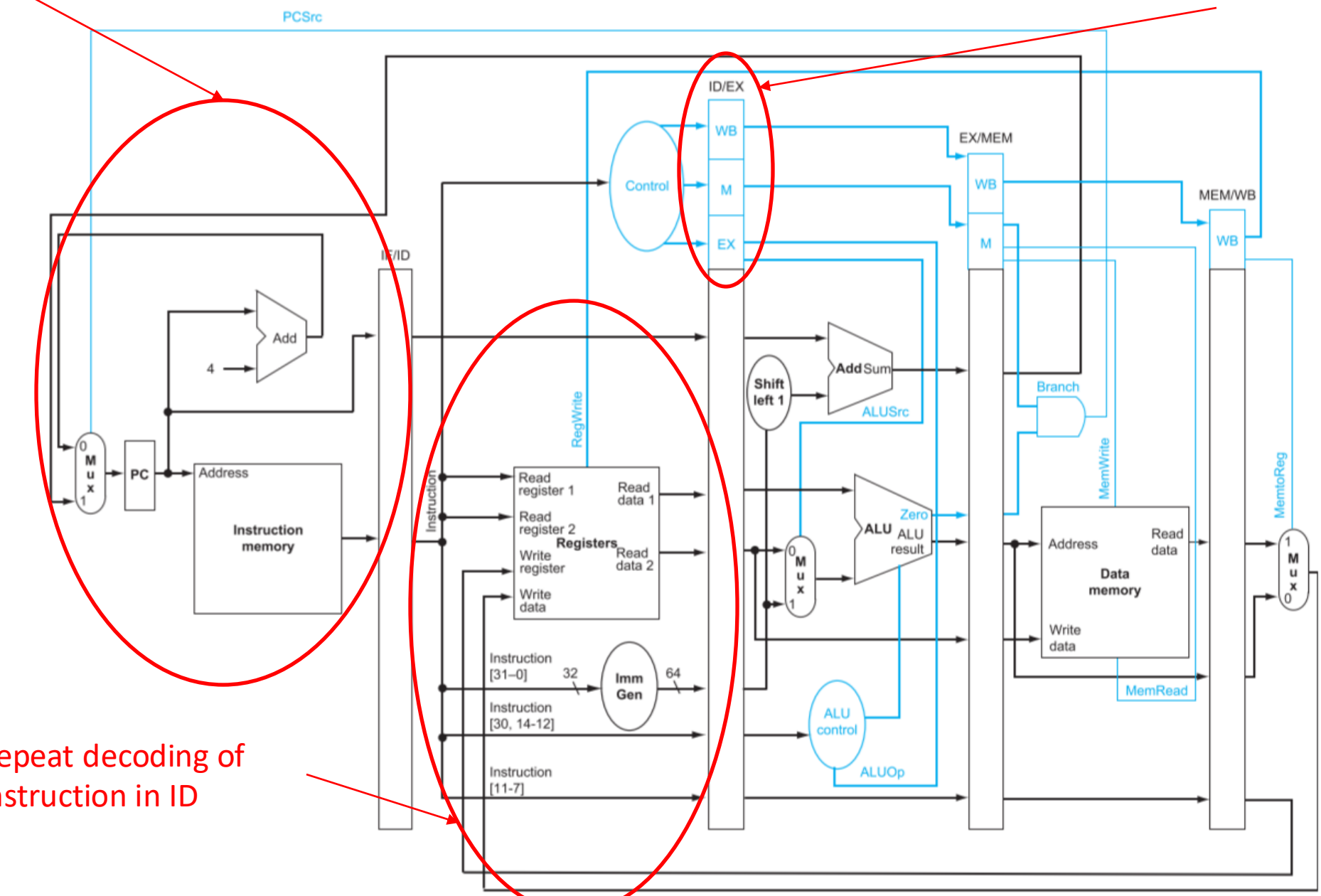




# Datapath with Hazard Detection

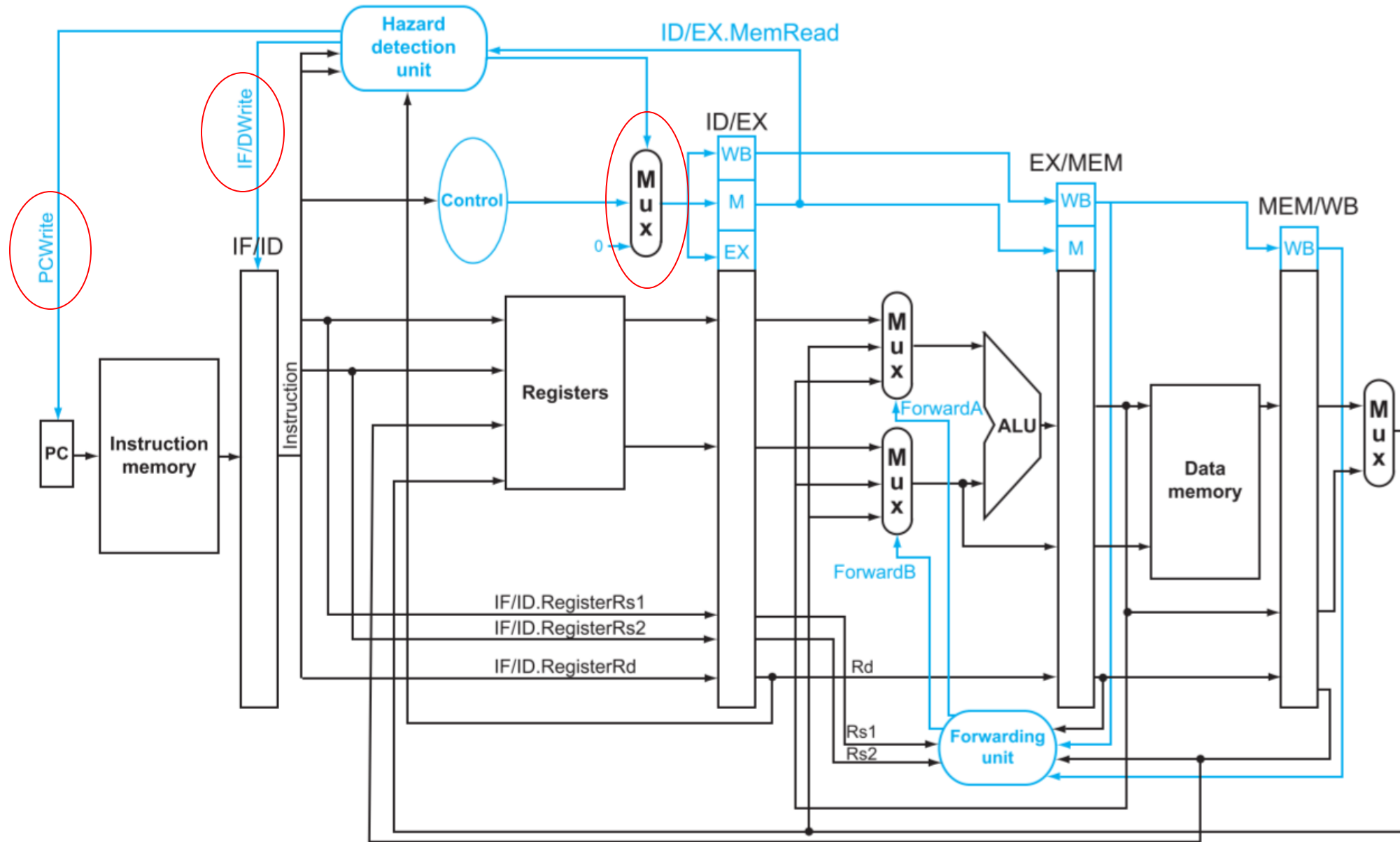

# Stall/Bubble in the Pipeline

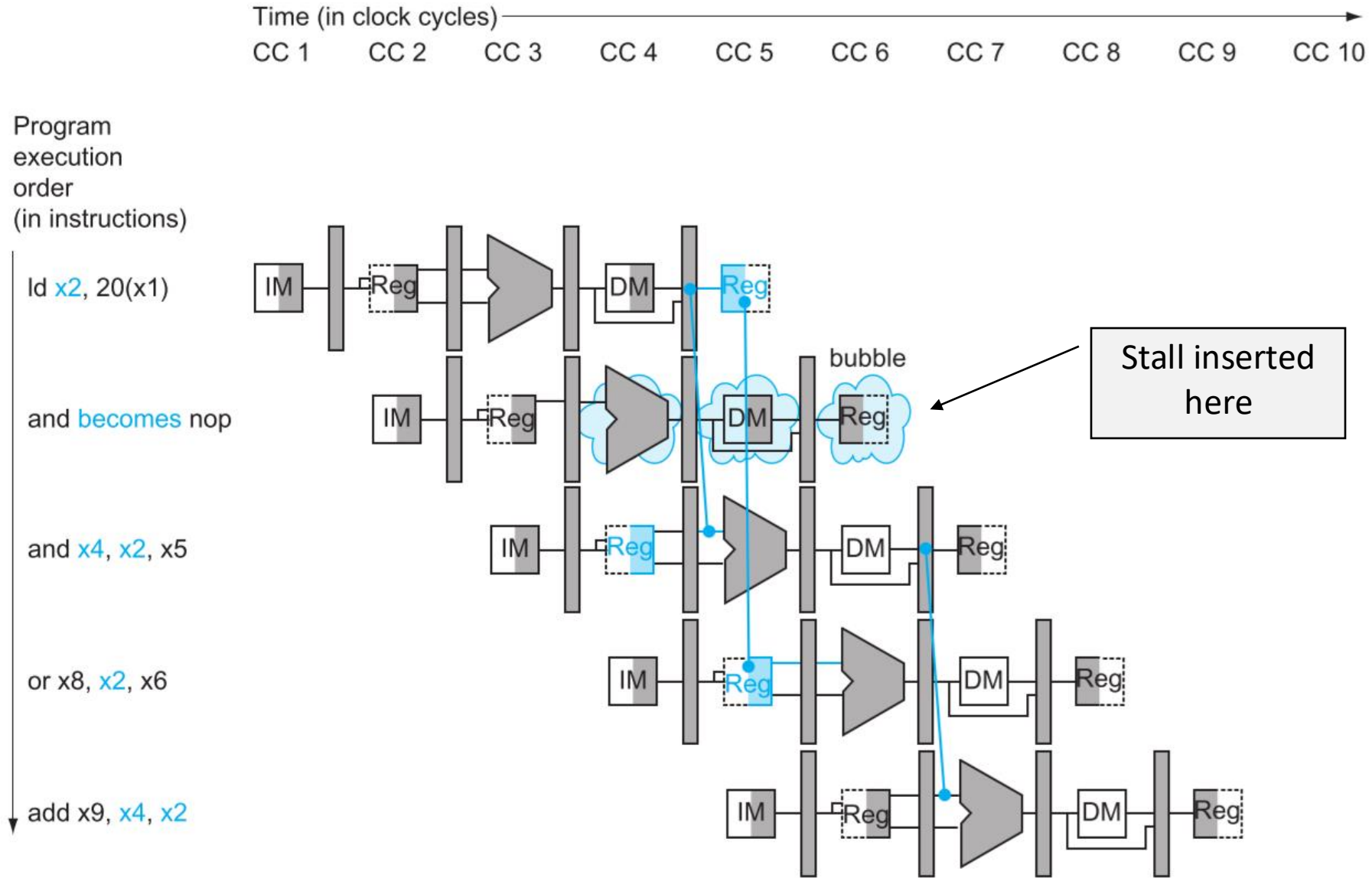

# Stall/Bubble in the Pipeline

